

EE 240B – Spring 2019

Advanced Analog Integrated Circuits

Lecture 4: Gain-Bandwidth Design




Ali Niknejad
Dept. of EECS

Preliminaries


- **This will be the first in a series of design methodologies we will develop**
 - To keep the discussion manageable, will generally assume that only a couple of specifications are critical C_0, W_0
 - And that all other specs will “automatically” be met
 - In practice, can inspect specs and technology capabilities to figure out which constraints are really active, and utilize the appropriate methodology
- **Will largely ignore biasing details for now**
 - But will patch this later

CS Amplifier Design Methodology

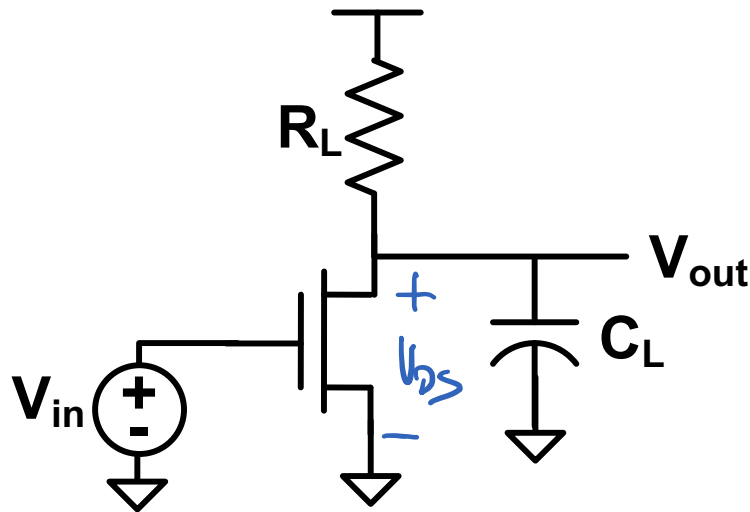

- **Input specifications:**
 - Minimum small signal gain A_v
 - Minimum 3dB bandwidth ω_{bw}
 - Fixed capacitive load C_L
 - Supply voltage V_{dd}
- **Goal: minimize power**
- **What are our design variables?** V_{DS}, R_L
 $W, L, V^*(V_{GS})$

Small Signal Model and Analysis

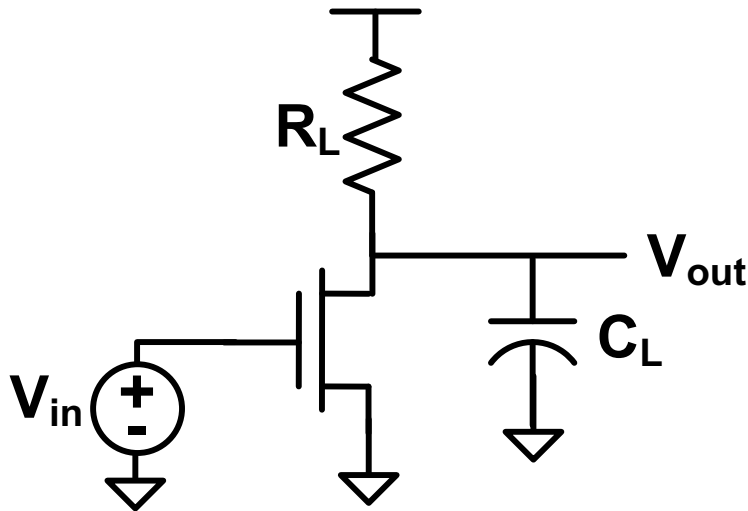

$$A_v = g_m R_L$$

$$= \frac{2 I_D}{V_{th}} R_L$$

$$R_L = \frac{A_v V_{th}}{2 I_D}$$

$$\omega_o = BW \approx \frac{1}{R_L C_L}$$

$$\omega_u = \omega_o \cdot A_v = \left(\frac{2 I_D}{A_v V_{th}} \right) \frac{1}{C_L}$$

Power and g_m

• Pick V^* $\Rightarrow I_D = \frac{g_m V^*}{2}$

• V_{DD} fixed

$$P = V_{DD} \cdot I_D$$

$$= \frac{g_m V_{DD} V^*}{2}$$

$$\omega_n = \frac{g_m}{C_L} = A_v \cdot \omega_o$$

$$P = \frac{A_v \omega_o (V_{DD} V^*) C_L}{2}$$

First Pass Methodology

- Pick V^* , L

$$I_D = \frac{g_m V^*}{2}$$

$$L_{\min} \text{ --- } L_{\max}$$

$$V_{\min}^* \text{ --- } V_{\max}^*$$

- $$g_m = A_v \omega_0 C_L$$

$$V^* \rightarrow V_{GS} \rightarrow J \downarrow W$$

- V_{GS} & $W \rightarrow$ LUT/BAG GRAPHS

- CALC $R_L = \frac{A_v}{g_m} = \frac{1}{\omega_0 C_L}$

Side Discussion: Digital vs. Analog Power

$$P_{digital} = \alpha_{0 \rightarrow 1} C_L V_{DD}^2 f_{clk}$$

↑

$$P_{analog} = \frac{1}{2} C_L V_{DD} V^* A_v \omega_{bw}$$

- What needs to be true for analog to be lower power than digital?

$$A_v \simeq 2$$

$$C_L \sim C_L$$

$$\omega_{bw} \cong 2\pi f_{clk}$$

$$\sim \alpha C_L V_{DD}^2 f_{clk}$$

$$\sim C_L V_{DD} V^* \underbrace{2\pi f_{clk}}$$

Relate Drain Cap to Gate Cap


$$C_{gs} = \frac{2}{3} W \cdot L \cdot C_{ox} = \frac{2}{3} W \cdot \underset{\substack{\uparrow \\ \text{(fixed)}}}{L} \cdot \frac{\epsilon_{ox}}{t_{ox}} \propto \textcircled{W}$$

$$C_{dd} = C_{gd} + C_{db}$$

$$= \textcircled{W} \cdot \delta L \cdot C_{ox} + \textcircled{C_{db}} \propto W$$

$$C_{db} = W \cdot L_j \cdot \frac{\epsilon_{si}}{x_{dep}}$$
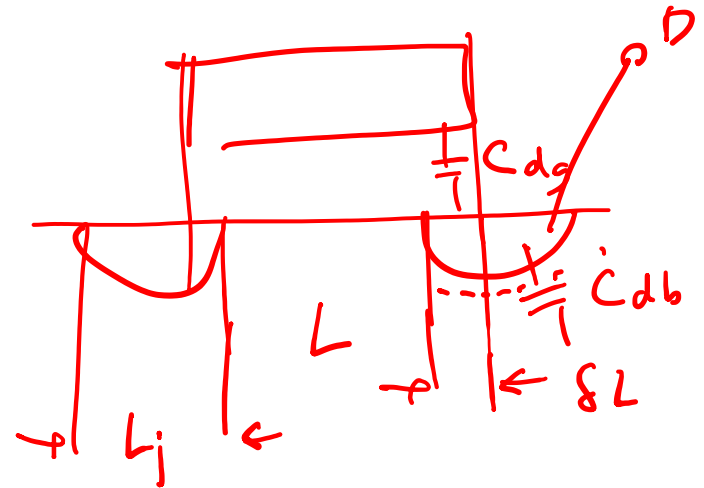
$$\frac{C_{dd}}{C_{gs}} = \frac{\left(\frac{\delta L}{L}\right) C_{ox} + \frac{L_j}{L} \frac{\epsilon_{si}}{x_{dep}}}{\frac{2}{3} \cdot \cancel{W} \cdot C_{ox} (1 + \mu)}$$



$$\mu = \frac{\delta L}{L} = \frac{C_{gd}}{C_{gs}}$$


$$\boxed{C_{dd} = \delta C_{gs}}$$

g_m vs. GBW revisited (1)

- Neglected C_{dd}

$$A_v \cdot \omega_o = \frac{g_m}{C_L + C_{dd}}$$

↑

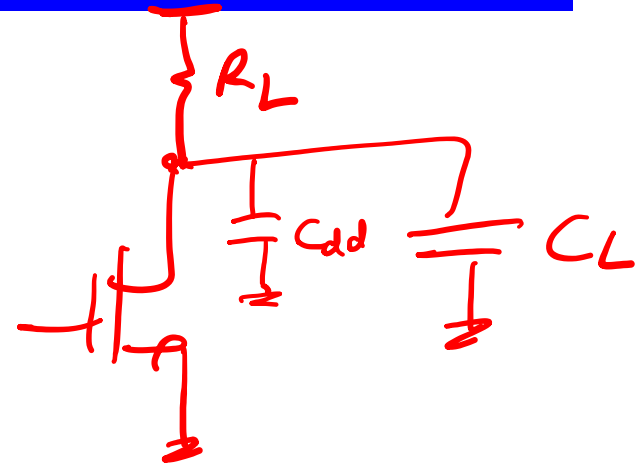

g_m vs. GBW revisited (2)

$$\frac{g_m}{C_{gg}} = \omega_T \quad C_{dd} = \beta C_{gg}$$

$$C_{dd} = \frac{\beta g_m}{\omega_T}$$

$$\frac{g_m}{C_L + C_{dd}} = A_v \cdot \omega_o = \frac{g_m}{\left(C_L + \frac{\beta g_m}{\omega_T (V^*)} \right)}$$

Solve for g_m

g_m vs. GBW revisited (3)

$$g_m = A_v \omega_o C_L + \frac{j A_v \omega_o}{\omega_T} g_m$$


$$g_m \left(1 - \frac{j A_v \omega_o}{\omega_T} \right) = A_v \omega_o C_L$$

$$g_m = \frac{A_v \omega_o C_L}{1 - \frac{j A_v \omega_o}{\omega_T (1^*)}}$$

Direct Implication


$$I_D = \frac{1}{2} \left(\frac{A_V \omega_{bw} V^* C_L}{1 - A_V \omega_{bw} / (\omega_T / \gamma)} \right)$$

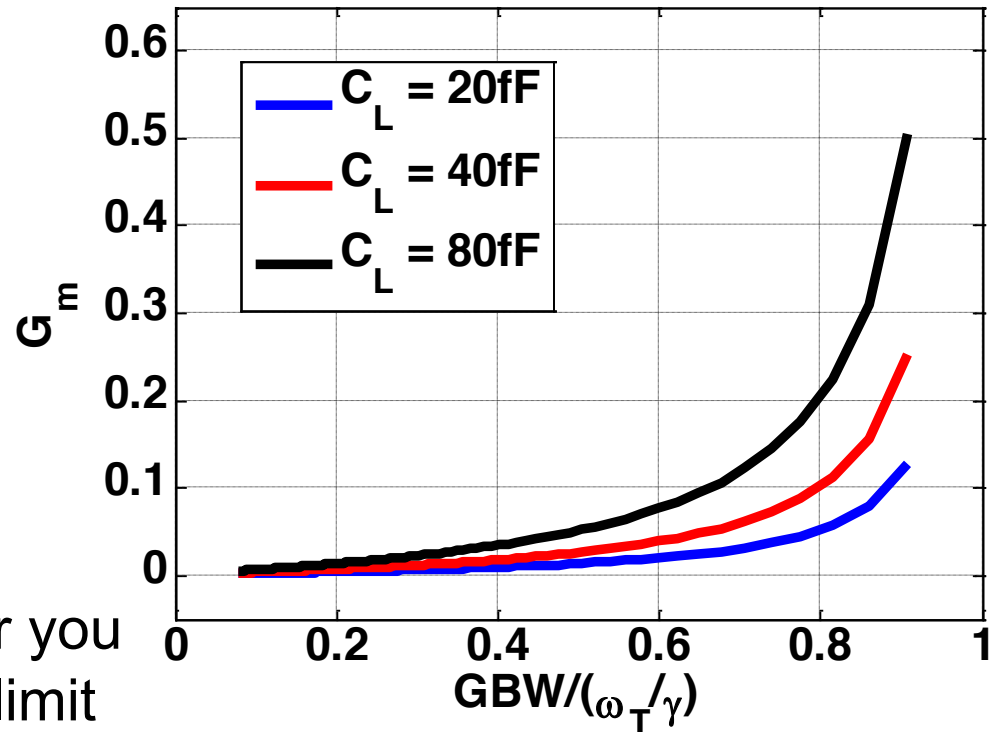- For a given V^* , there is a maximum GBW you can achieve
 - No matter how much power you spend, cannot exceed this limit (with this topology)



$$A_V \omega_0 = \frac{\omega_T}{\gamma} \Rightarrow \text{infinite power}$$

Methodology Take 2

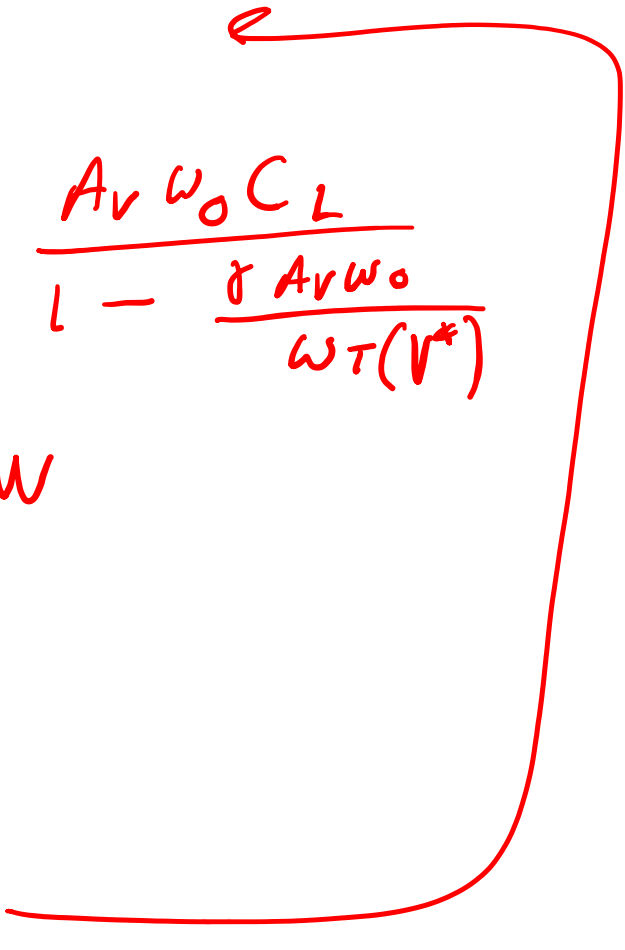- (1) Pick V^* , L
 - (2) Compute $g_m = \frac{A_v \omega_0 C_L}{1 - \frac{\gamma A_v \omega_0}{\omega_T(V^*)}}$
 - (3) Find V_{GS} & W
 - (4) $R_L = \frac{1}{\omega_0 C_L}$
 - (5) Adjust V^* , L
- 
- with power

Methodology Take 2`

(1) Pick L

$$I_D = \frac{1}{2} g_m V^* = \frac{1}{2} \frac{A_v \omega_0 C_L}{1 - \frac{\gamma A_v \omega_0}{\omega_T(V^*)}} \times V^*$$

(2) $\min \left(\frac{V^*}{1 - \frac{\gamma A_v \omega_0}{\omega_T(V^*)}} \right) \rightarrow \text{Sweep } V^*$

(3) $V^* \rightarrow V_{GS} \rightarrow W$

(4) Set $R_L = \frac{A_v}{g_m}$

What about r_o ?

$$A_v = g_m (r_o \parallel R_L)$$


$$A_v = g_m \frac{r_o R_L}{r_o + R_L} = \frac{a_o R_L}{\frac{a_o}{g_m} + R_L}$$

$$A_v \left(\frac{a_o}{g_m} + R_L \right) = \frac{a_o R_L}{A_v}$$

$$R_L \left(\frac{a_o}{A_v} - 1 \right) = \frac{a_o}{g_m}$$

$$R_L = \frac{a_o / g_m}{\frac{a_o}{A_v} - 1} = \frac{A_v / g_m}{1 - \underbrace{\frac{A_v}{a_o}}_{V_{DS} \text{ BIAS}}}$$

Bias Point

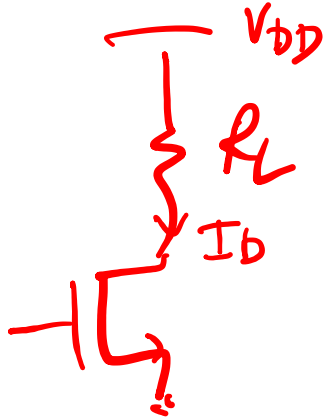

$$V_{DS} = V_{DD} - I_D R_L$$

$$= V_{DD} - \frac{g_m V^*}{2} R_L$$

$$= V_{DD} - \frac{\frac{g_m V^*}{2} \frac{A_v}{g_m}}{1 - \frac{A_v}{a_o}}$$

$$V_{DS} = V_{DD} - \frac{V^* A_v}{2(1 - A_v/a_o)}$$

$$a_o = f(V_{DS})$$

pick $a_o(\text{mid rail})$

$$V_{DS} \rightarrow a_o(V_{DS}) \rightarrow V_{DS}'$$

$$V_{DS}' \leftarrow a_o(V_{DS}')$$