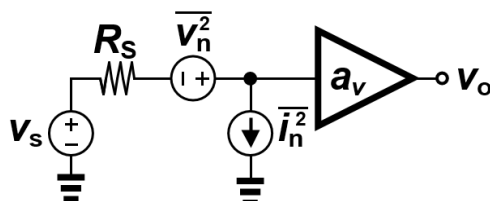


Problem Set 2
Due Fri Feb 22, 2019
Submit through bCourses

1. Electronic Noise.

You are given two amplifiers modeled by the circuit below. Both amplifiers have the same gain a_v but different input referred noise (Table 1) and are otherwise ideal. The amplifiers are driven by a resistive voltage source R_S .



Noise source	Amplifier A	Amplifier B
$\sqrt{\frac{v_n^2}{\Delta f}}$	$1 \frac{\text{nV}}{\sqrt{\text{Hz}}}$	$10 \frac{\text{nV}}{\sqrt{\text{Hz}}}$
$\sqrt{\frac{i_n^2}{\Delta f}}$	$1 \frac{\text{pA}}{\sqrt{\text{Hz}}}$	$1 \frac{\text{fA}}{\sqrt{\text{Hz}}}$


- (a) Calculate the input referred voltage noise in $\text{V}/\sqrt{\text{Hz}}$ achieved with the two amplifiers, respectively. Report your result in Table 2 below. You may assume that the amplifier voltage and current noise sources are uncorrelated (usually not the case).

R_s	Amplifier A	Amplifier B
50Ω		
$5 \text{ M}\Omega$		

- (b) Briefly comment on the significance of your result.

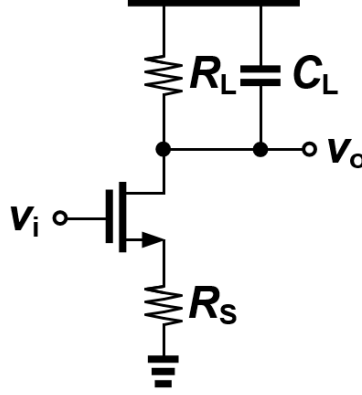
2. Amplifier Noise.

For the amplifier shown below, derive analytical expressions as a function of g_m , γ , f_T , R_L , R_S , and C_L .




- (a) The voltage gain $a_v(s) = v_o/v_i$
- (b) The PSD of the noise in $V/\sqrt{\text{Hz}}$ at node v_o
- (c) The total noise integrated over all frequencies at node v_o
- (d) The dynamic range of the circuit as a function of the peak-to-peak voltage range $V_{o,pp}$ at node v_o
- (e) The minimum detectable signal in $\text{nV}/\sqrt{\text{Hz}}$ at low frequency and μV_{rms} based on the total noise at the output of the amplifier.
- (f) Comment on the effect of R_s on the dynamic range and minimum detectable signal of the circuit.
- (g) Find the component values that meet the following requirements: $a_{vo} = -5$, a 3-dB bandwidth at v_o of 500-MHz, $\gamma = 1$, $V^* = 150\text{mV}$, $f_T = 50\text{GHz}$, 50-dB dynamic range at v_o , $V_{o,pp} = 500\text{mV}$, $R_s = 500$ and minimum power dissipation.
- (h) Verify your result from part (g) with SPICE. Model the transistor as an ideal transconductor with input capacitance C_{GS} and a drain current noise source. Model the transistor as an ideal transconductor with gate-to-source capacitance and drain current noise. Assume infinite output resistance.

3. Noise Cancelling Amplifier

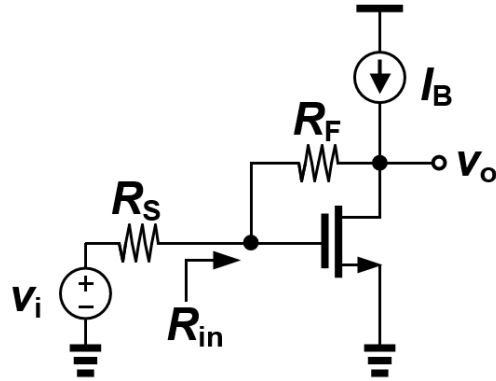

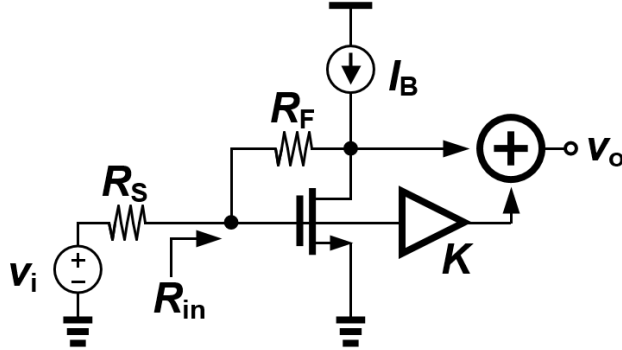- Find the input impedance R_{in} .
- What is the output noise under the constraint of impedance matching ($R_{in} = R_S$)? Ignore noise from current source I_B .
- What is the output noise with the modified topology below, under a matching condition? How would you pick the value of K ? Is K positive or negative?



- Replace the functional block above with real circuit, and re-calculate output noise.