

EE 240B – Fall 2019


Advanced Analog Integrated Circuits

Lecture 8: Operational Transconductance Amplifiers (II)



Ali M. Niknejad
Dept. of EECS

Closer Look at Cascode Dynamics

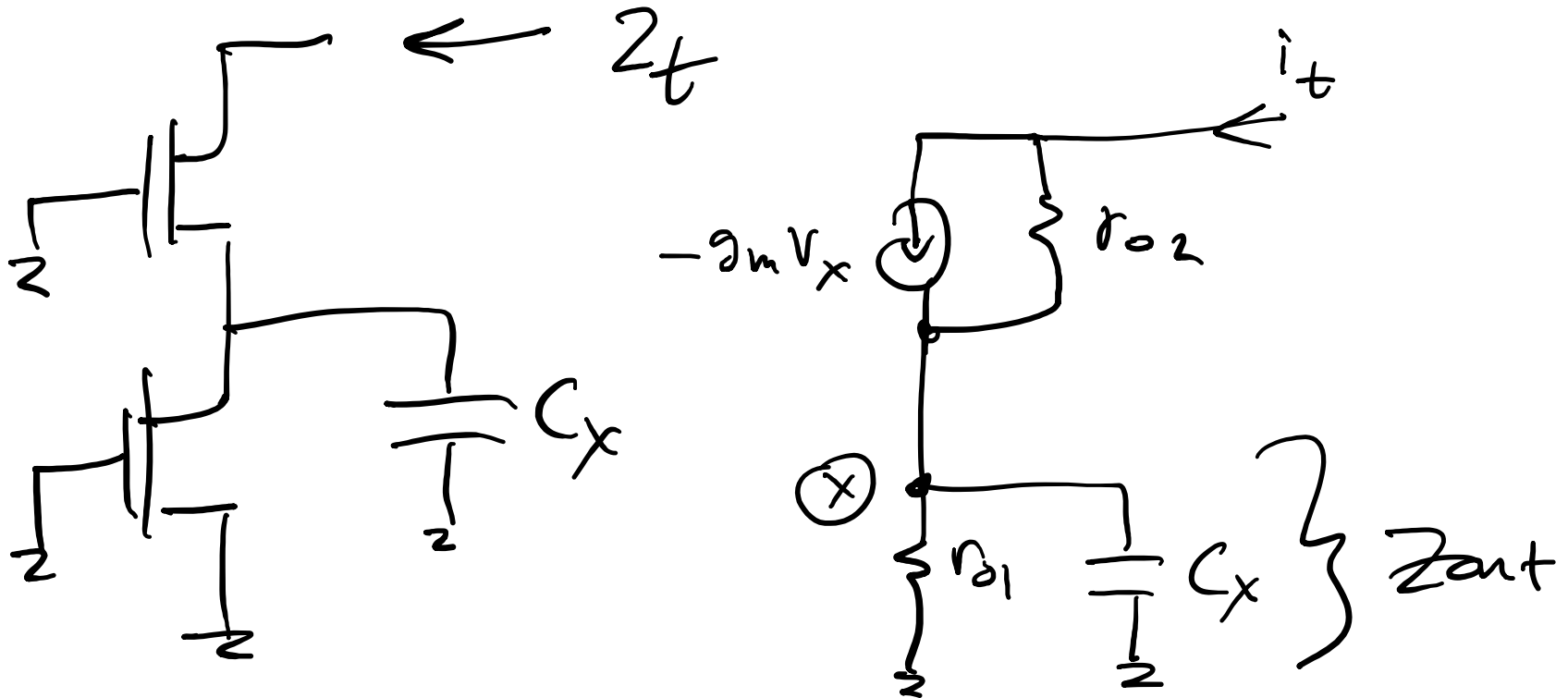


$$V_t = i_t \cdot Z_{out} + (i_t + g_m \underbrace{V_x}_{i_t Z_{out}}) r_{o2}$$

$$V_t = i_t \left(Z_{out} + r_{o2} + g_m \frac{i_t Z_{out}}{i_t} \cdot r_{o2} \right)$$



Cascode Z_{out} vs. f
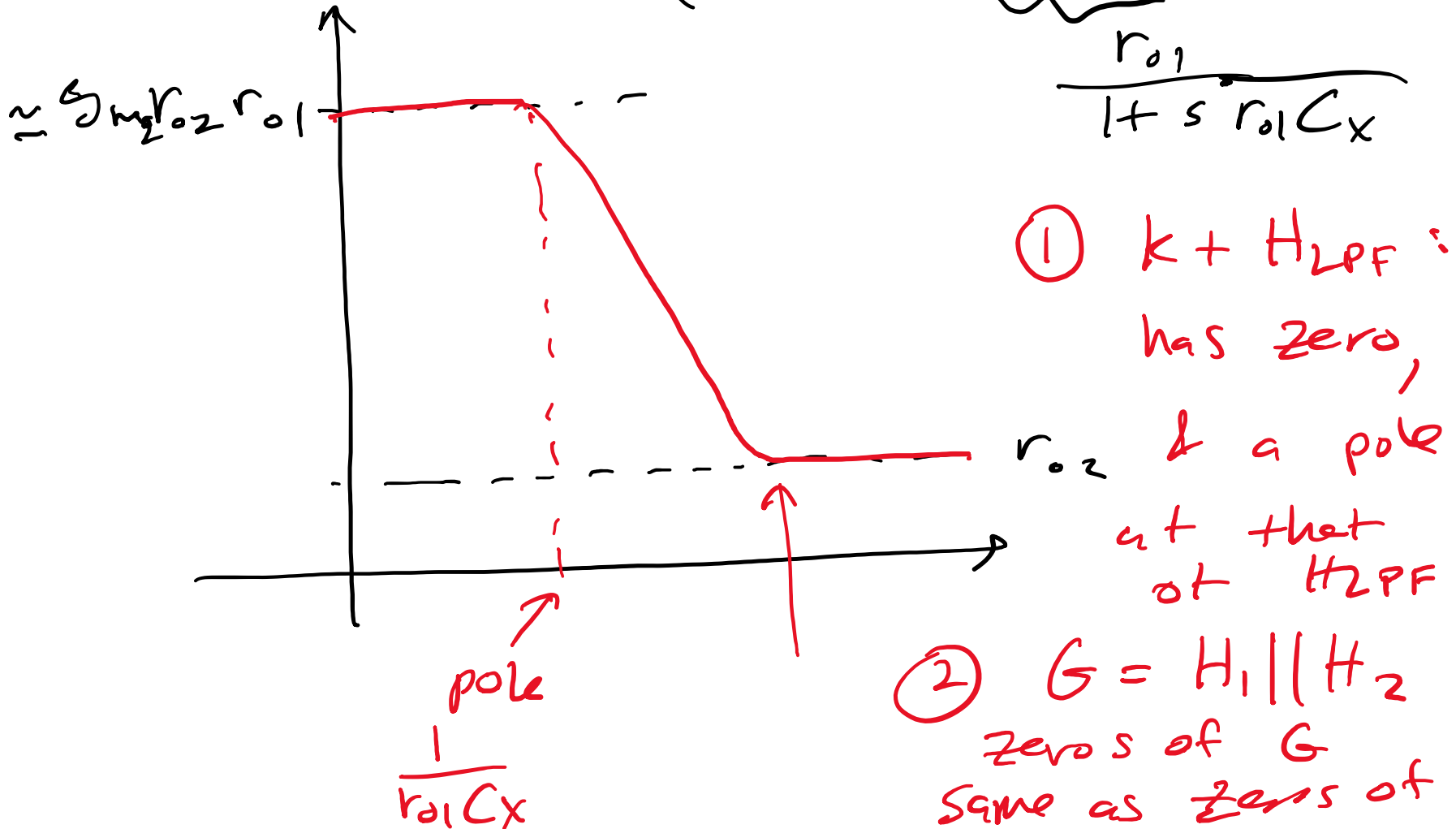
$$Z_t = r_{o2} + (g_{m2}r_{o2} + 1) \underbrace{Z_{out}}_{\frac{r_{o1}}{1 + s r_{o1} C_x}}$$




Load + Cascode Z_{out} vs. f
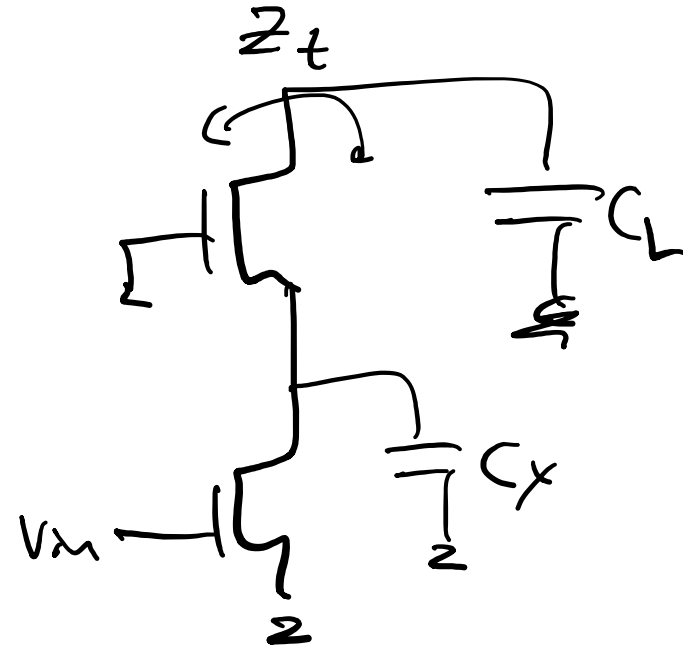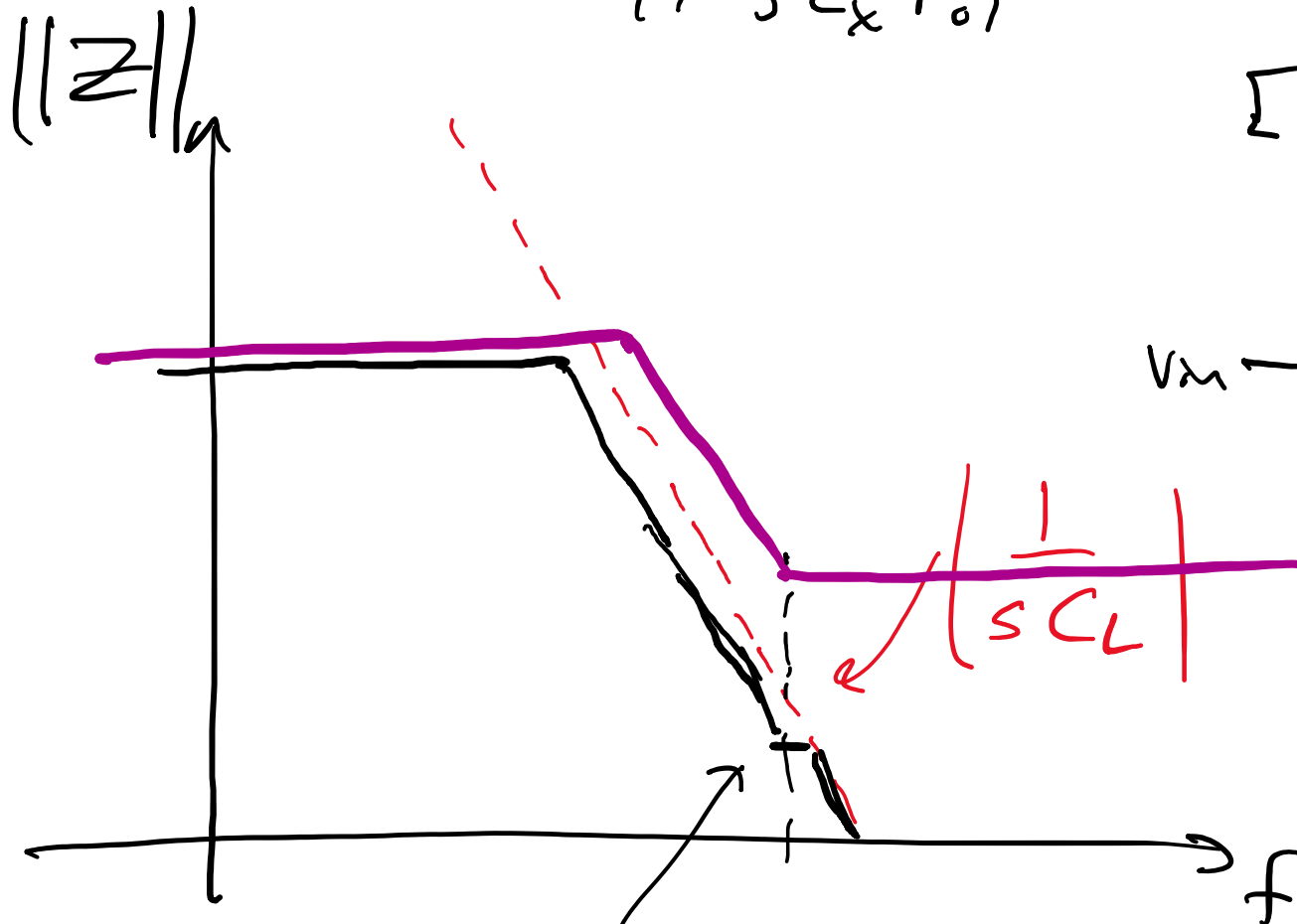
$$Z_t = r_{o2} + \frac{r_{o1}(1 + g_m r_{o2})}{1 + s C_x r_{o1}}$$



Pole-Zero Doublets

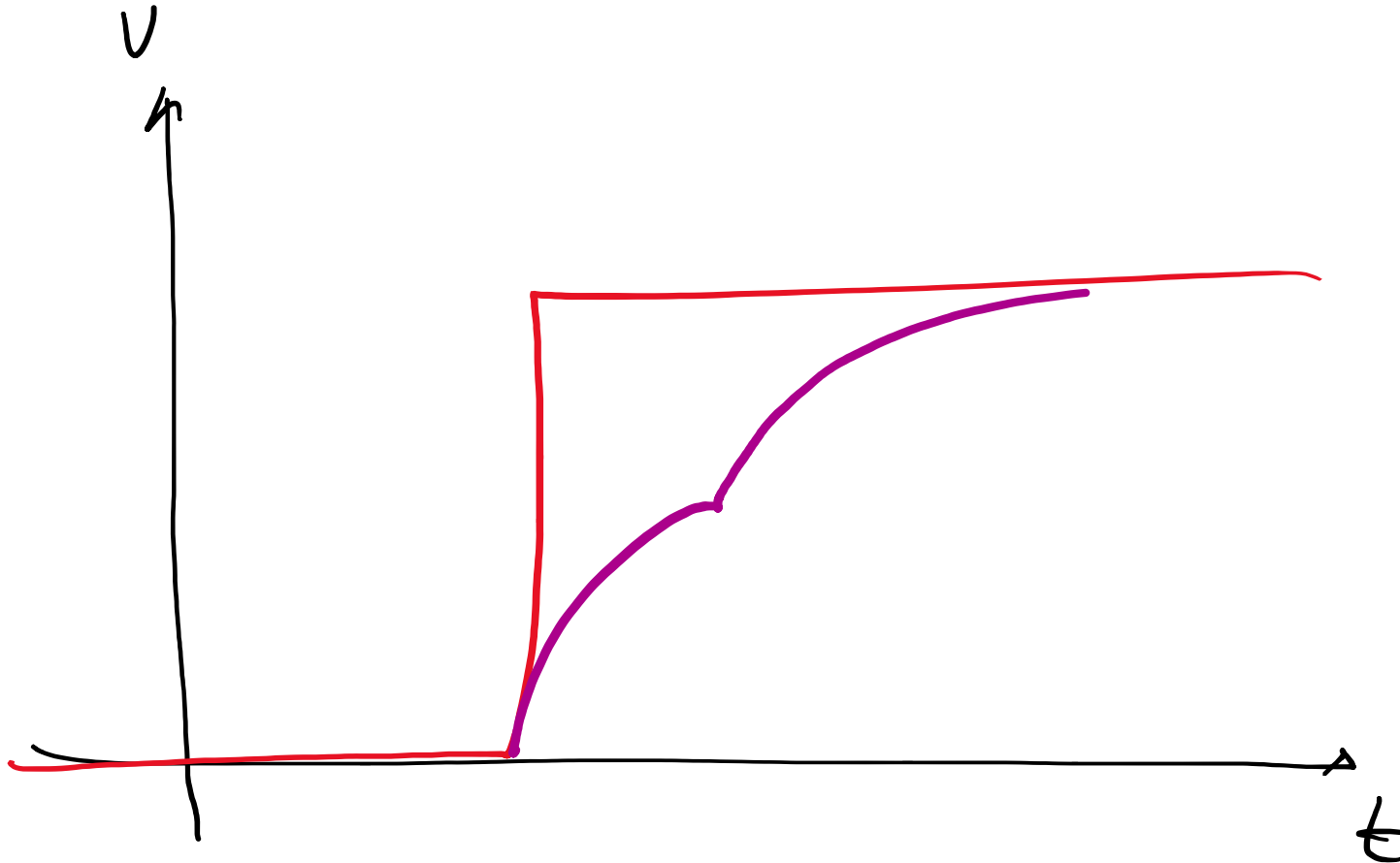

Discussion


- **Doublet generally not important in “simple” cascode since it shows up at high frequencies**
- **But, doublets can show up in similar circuits**
 - In particular, when you try and increase the gain beyond what a simple cascode can support

Openloop Gain : *price is swing!*

$$a_{vo} = g_m R_o$$


costs power
→ set by dynamics

“boost” R_o to get
sufficient gain

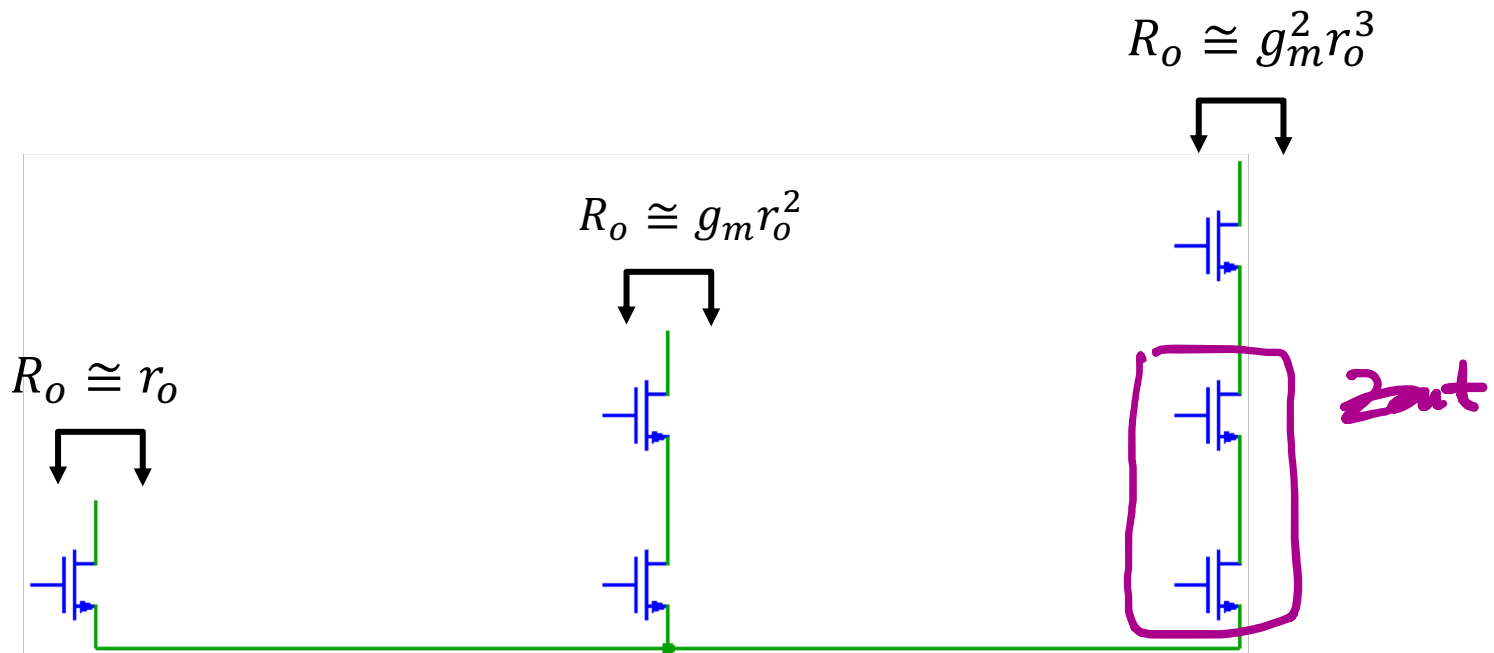

Gain Boosting

$$R_o \cong r_{o1} g_{m2} r_{o2} a_o$$

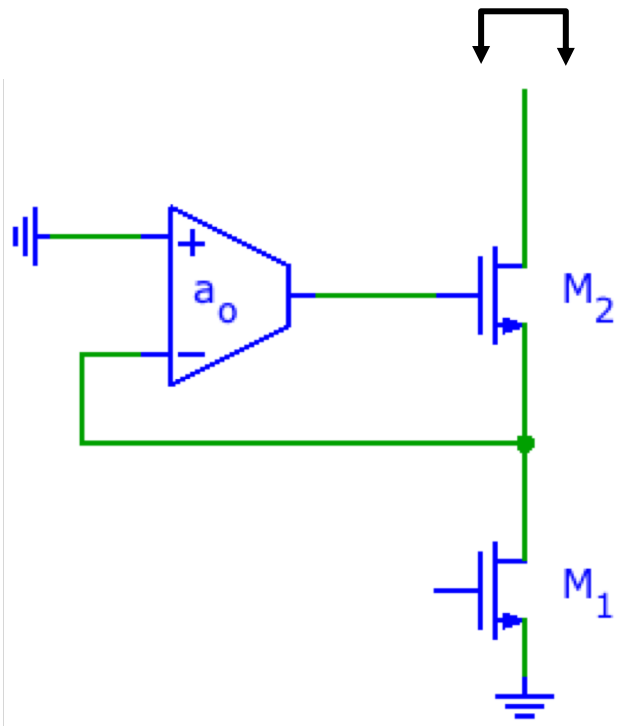


$$R_o = (G_m r_{o2}) r_{o1} = a_o g_{m2} \cdot r_{o1} \cdot r_{o2}$$

- **Use feedback to further increase R_{out}**

- No increase of V_{min} (unlike double cascode)

- **References:**

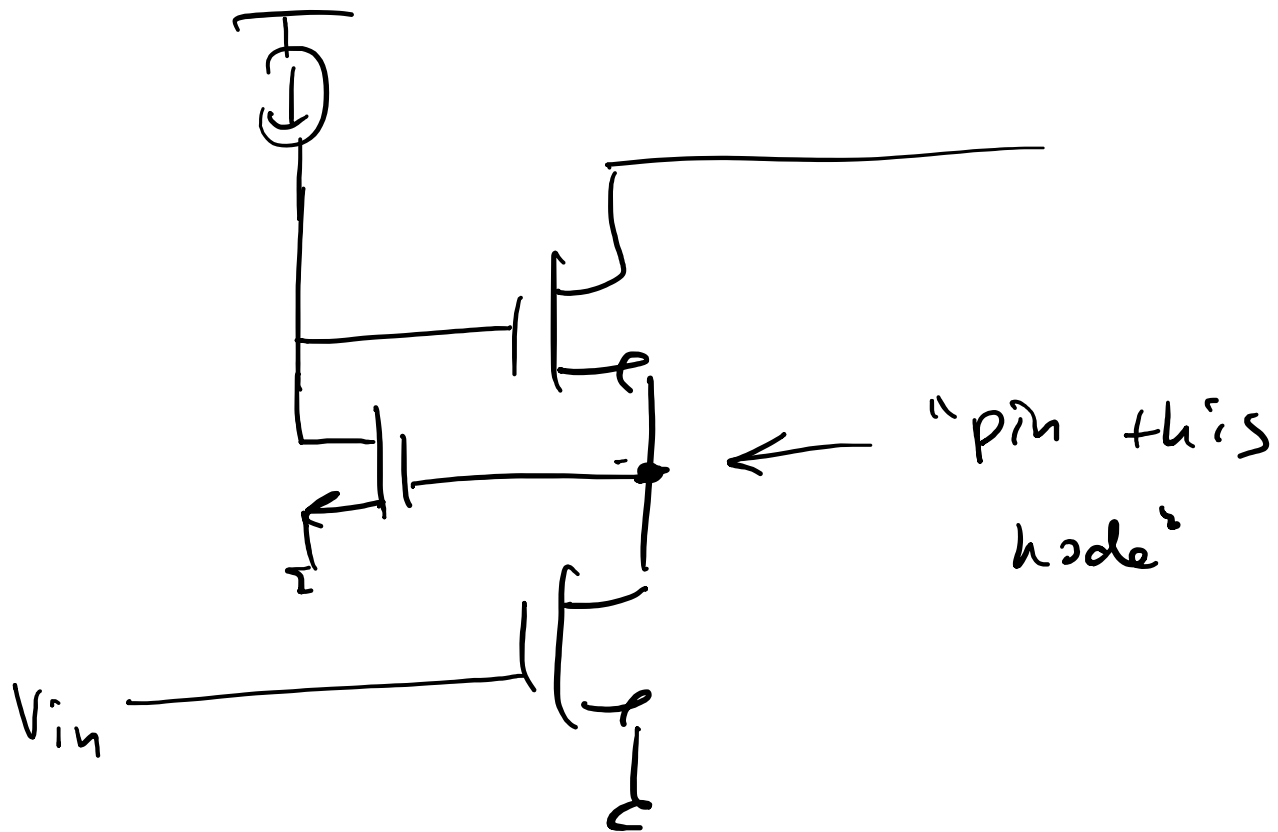- B. J. Hosticka, "Improvement of the gain of MOS amplifiers," JSSC, Dec. 1979 , pp. 1111-4.
- E. Sackinger and W. Guggenbuhl, "A high-swing high-impedance MOS cascode circuit", JSSC, Feb. 1990, pp. 289-298.
- K. Bult, G. Geelen, "A fast-settling CMOS op-amp for SC circuits with 90-dB DC gain," JSSC, Dec. 1990 , pp. 1379-84.




High Frequency Analysis

- Loop gain $|T|=1 @ \omega \approx \frac{g_m}{C_2}$

$$T(s) = \frac{g_{m3}}{sC_2} \frac{1}{1 + s \frac{C_1}{g_{m2}}} = \frac{\omega_{u3}}{s} \frac{1}{1 + s \frac{C_1}{g_{m2}}}$$

- For acceptable phase margin
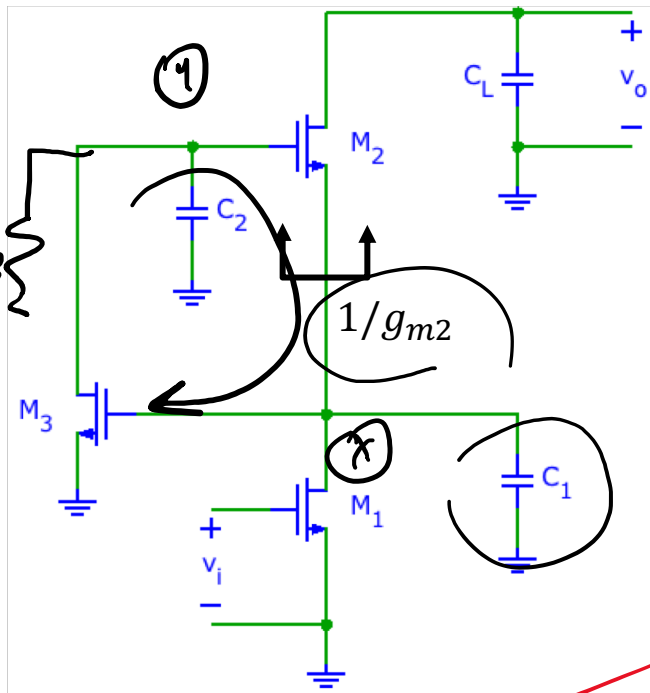
$$\frac{g_{m2}}{C_1} = \omega_{p2} > k\omega_{u3}$$



$$\textcircled{X} \quad p_1 \sim \frac{g_{m2}}{C_1}$$


$$\textcircled{1} \quad p_2 = \frac{1}{C_2 R_3} \quad \left. \vphantom{\frac{1}{C_2 R_3}} \right\} \text{dominant pole}$$

Overall Amplifier Response

$$\frac{v_o}{v_i} = \frac{g_{m1}}{sC_L} \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_o Q} + \frac{s^2}{\omega_o^2}}$$


$$\omega_z = \omega_{u3} \quad \omega_o = \sqrt{r}\omega_{u3} \quad Q = \frac{1}{\sqrt{r}}$$
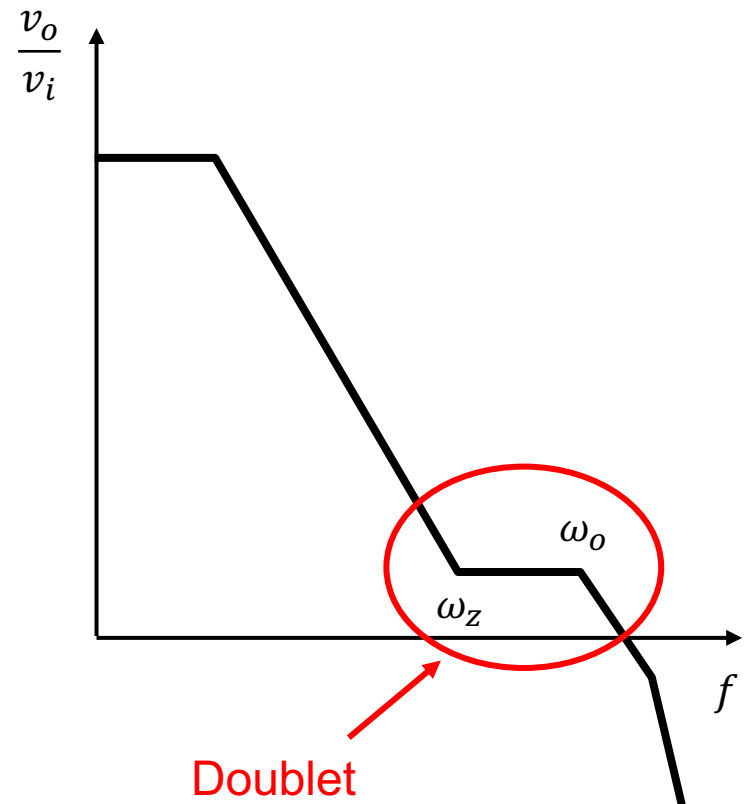
$$\text{for } Q < 0.5 \Rightarrow r > 4$$



Ref: M. Das, "Improved design criteria of gain boosted CMOS OTA with high-speed optimizations," IEEE CAS II, March 2002, pp. 204-7.

Graphical Derivation

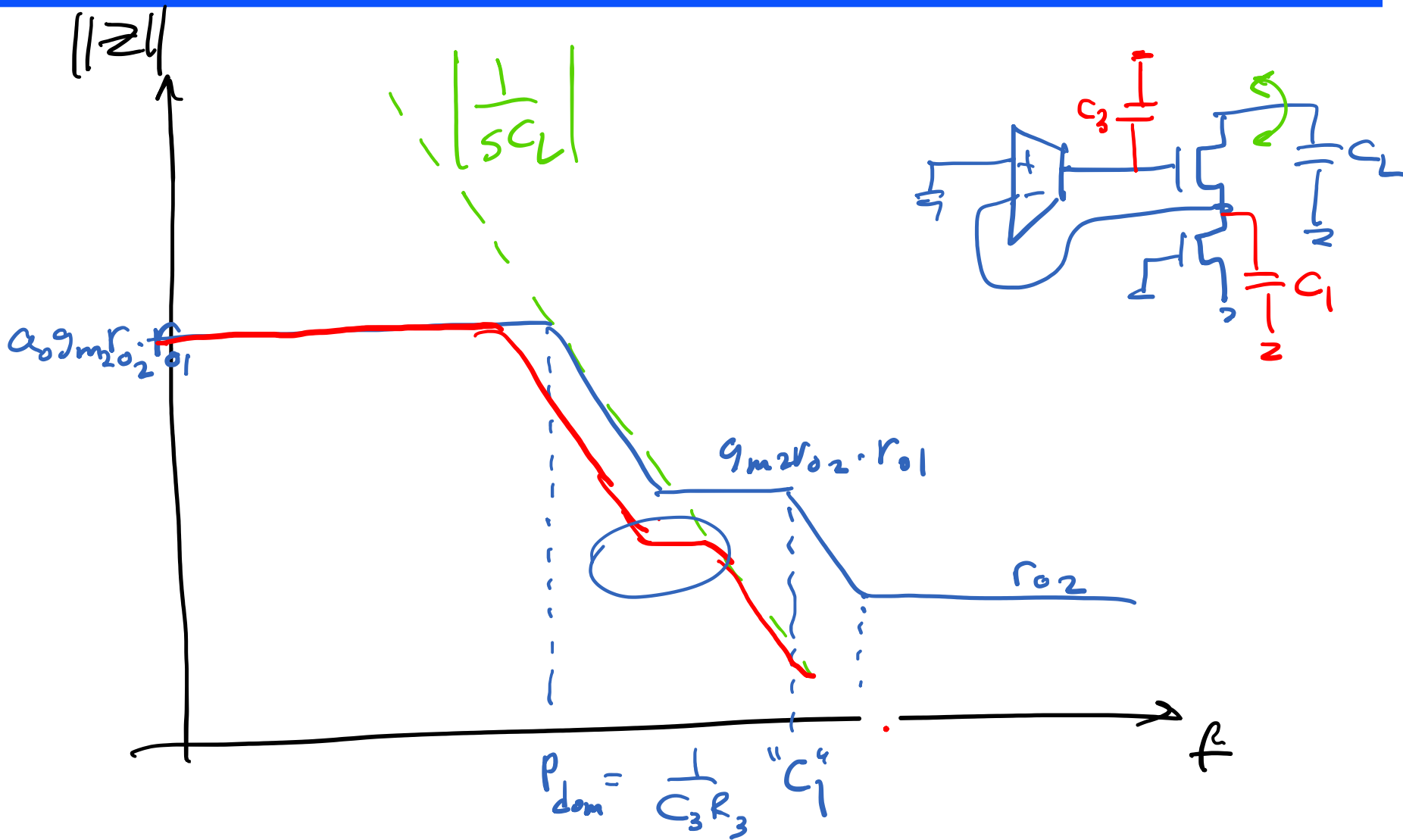

Pole-Zero Doublets

- Often "closely spaced"
 - May miss in Bode plot!
- Origins
 - Feedforward (e.g. Miller capacitance, C_{gd} , ...)
 - Frequency dependent degeneration (series feedback, e.g. cascode)
- Concerns
 - Ringing (if high Q)
 - Slow settling

Ref: Y. Kamath, R. G. Meyer, and P. R. Gray, "Relationship between frequency response and settling time of operational amplifiers," *IEEE J. Solid-State Circuits*, pp. 347–352, Dec. 1974.

Doublet Settling

- Amplifier model: replace G_{mo} with

$$G_m(s) = G_{mo} \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}} \quad \text{with} \quad \begin{aligned} \omega_p &= \beta \omega_{-3dB}, & \omega_{-3dB} & \text{ is bandwidth of } T(s) \\ \omega_z &= \frac{\omega_p}{\alpha} \\ \alpha &= 1 + \varepsilon & \text{ with } |\varepsilon| & \ll 1 \end{aligned}$$

- Closed-loop response

$$\frac{V_o}{V_{in}} = -c \frac{1}{1 + s \frac{C_{Leff}}{FG_m(s)}} \cong -\frac{c}{1 + \frac{s}{\omega_{-3dB}}} \left(\frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_{pp}}} \right) \quad \text{with} \quad \begin{aligned} \omega_{-3dB} &= \frac{FG_{mo}}{C_{Leff}} \\ \omega_{pp} &\cong \omega_p \end{aligned}$$

Notation from Y. Kamath, R. G. Meyer, and P. R. Gray, "Relationship between frequency response and settling time of operational amplifiers," *IEEE J. Solid-State Circuits*, pp. 347–352, Dec. 1974.

Doublet Step Response

$$v_{o,step}(t) = -cV_{step} \left(1 + Ae^{-t\omega_{-3dB}} + Be^{-t\omega_{pp}} \right)$$

with


$$A \cong -1$$

$$B \cong \varepsilon \frac{\beta}{1 - \beta^2}$$


↑
main amplifier

↑
doublet

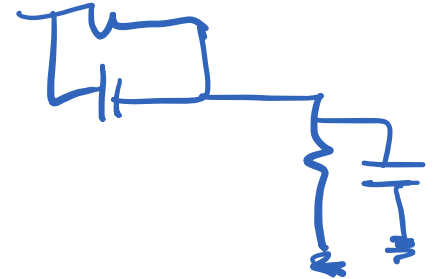
- Case A: $\omega_{pp} > \omega_{-3dB}$
 - Doublet settles faster than main amplifier
 - Has no impact on overall settling time (unless $B \gg A$)
- Case B: $\omega_{pp} < \omega_{-3dB}$
 - Doublet settles more slowly than main amplifier
 - Determines settling time unless $B \ll A$
 - Acceptable in “low precision” applications (e.g. oscilloscope probes)
 - Avoid when precise settling is required



Doublet Example

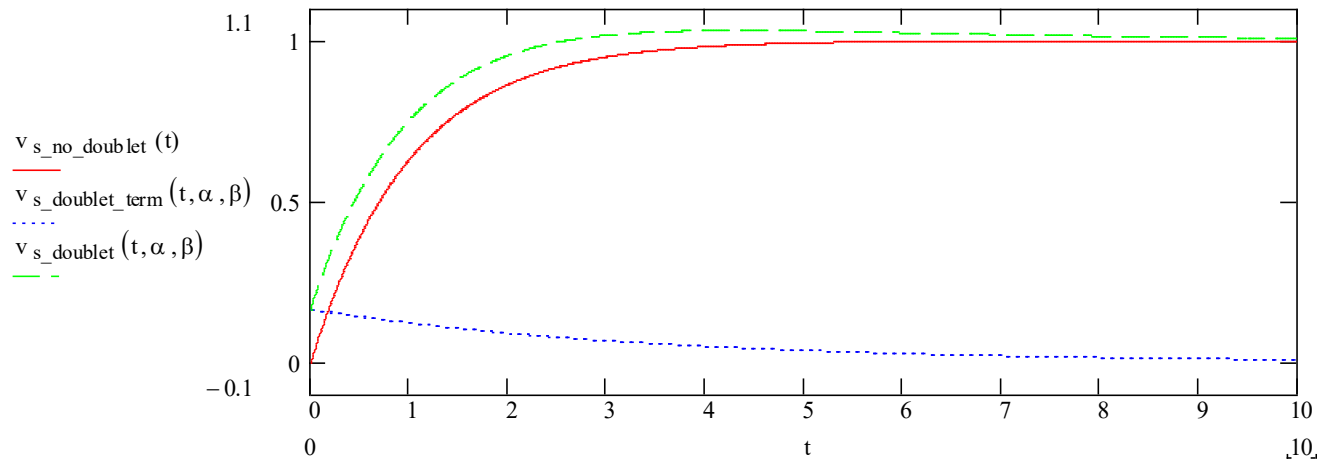

$$\alpha = 1.5$$
$$\beta = 0.3$$

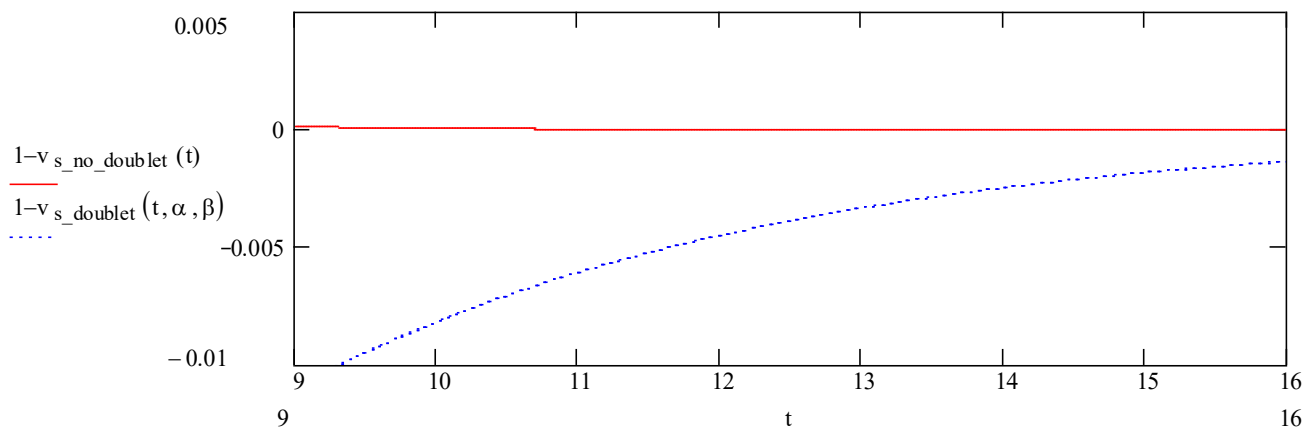

Gain Boosting – Doublets

- Doublet is near ω_{u3}

zero in $z \Rightarrow$ leads to doublet
- Stability:

amplifier gain/bandwidth

$$\omega_{u3} > \beta \left(\frac{g_{m1}}{C_{Ltot}} \right) \text{ for fast settling}$$

$$\omega_{u3} < \frac{g_{m2}}{C_1} \text{ (large } r)$$

parasitic pole of feedback loop
- Practical designs show 20-30% power penalty for booster
 - Since usually $C_2 < C_L$

If it works, do it again!

2144

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 39, NO. 12, DECEMBER 2004


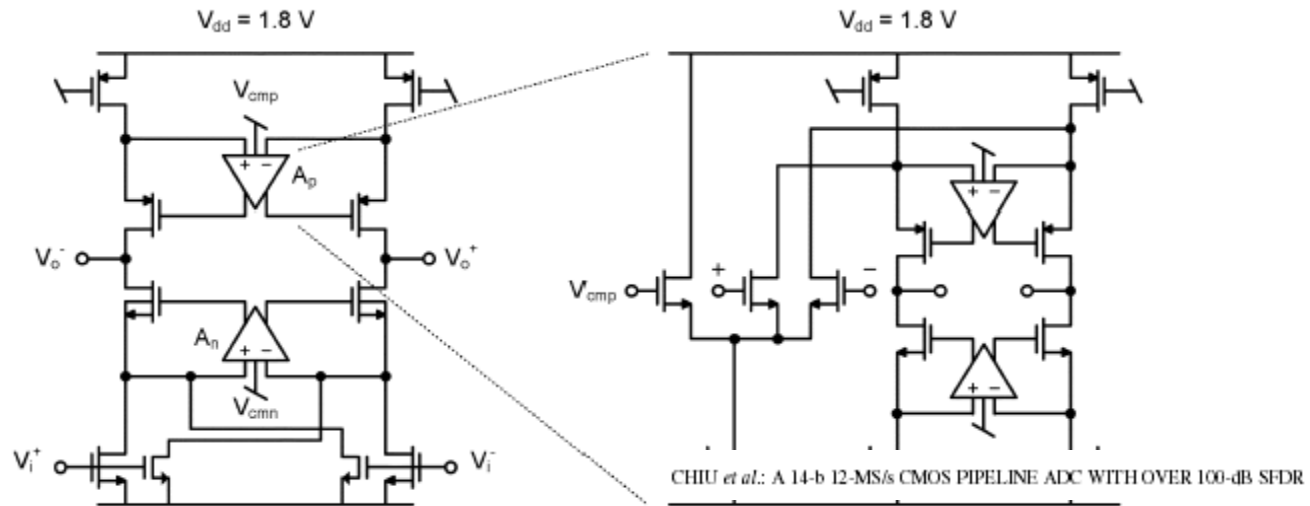


Fig. 8. Nested CMOS gain-boosting technique.

- Since in advanced scaled CMOS $g_m r_o$ is small, we can use nested gain boosting for higher output impedance.
- Watch out for pole-zero doublets!

Telescopic OTA: Common Mode vs. Swing

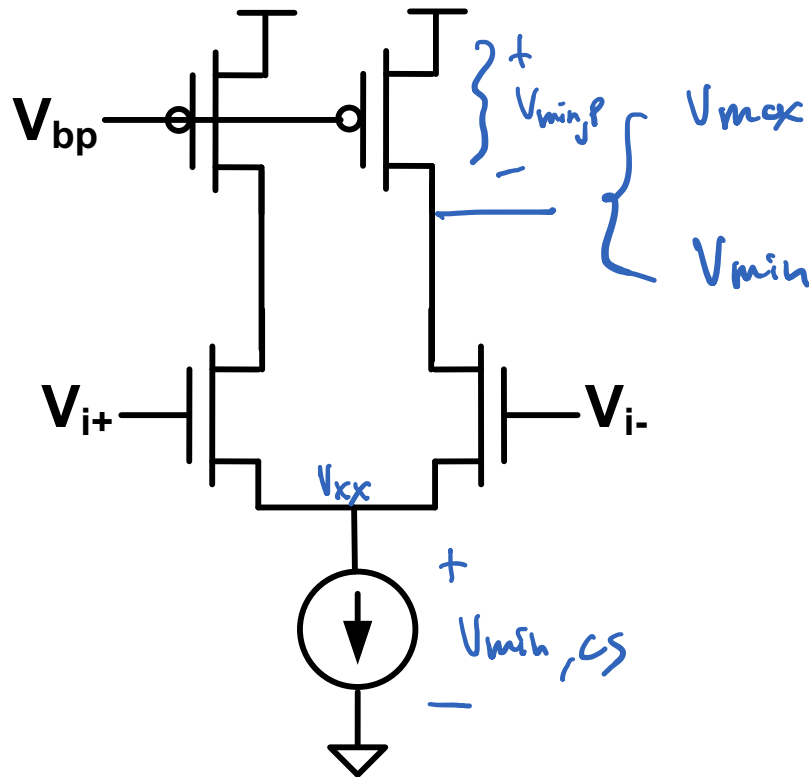

$$\underline{V_{max}} = V_{DD} - V_{min,p}$$


$$V_{min} = \text{set by CM}$$

$$V_{xx} = V_{CMi} - V_{th} - V_n^*$$

$$\underline{V_{min}} = V_{min,n} + V_{xx}$$


$$V_{sw} = V_{max} - V_{min}$$

Folded-Cascode Schematic

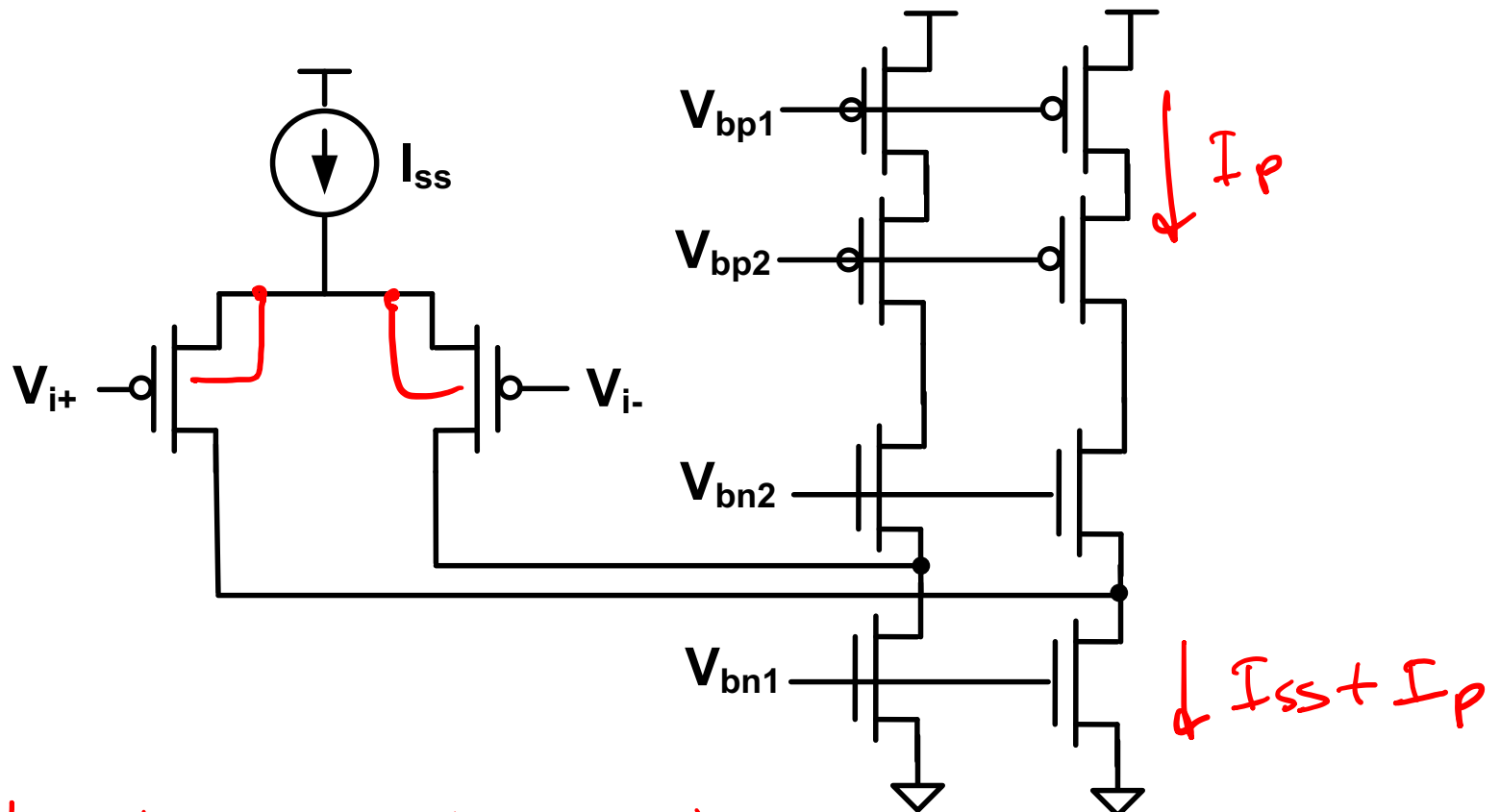


Input CM does not affect output swing


Folded-Cascode Noise

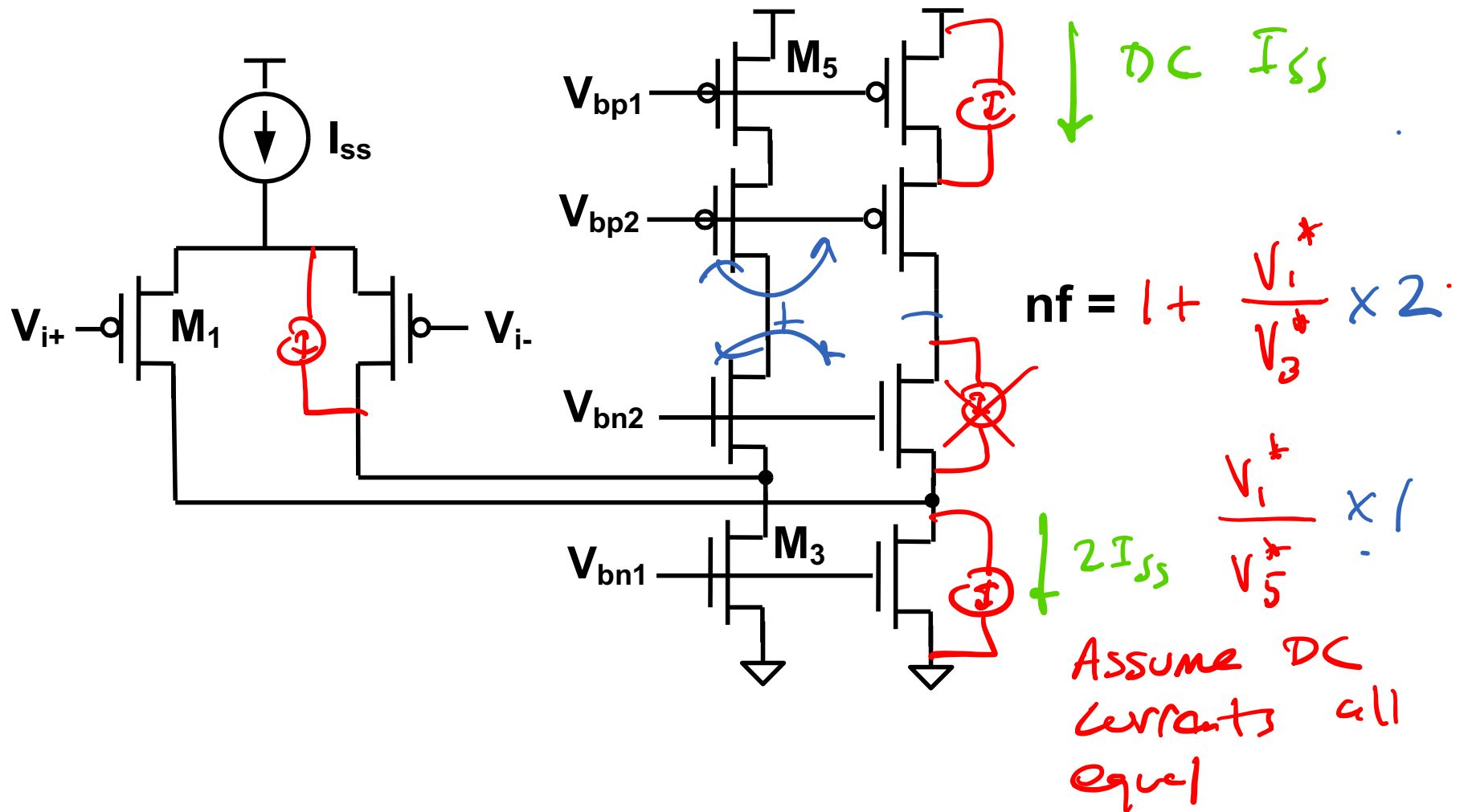

Low Frequency Gain: a_v and A_v

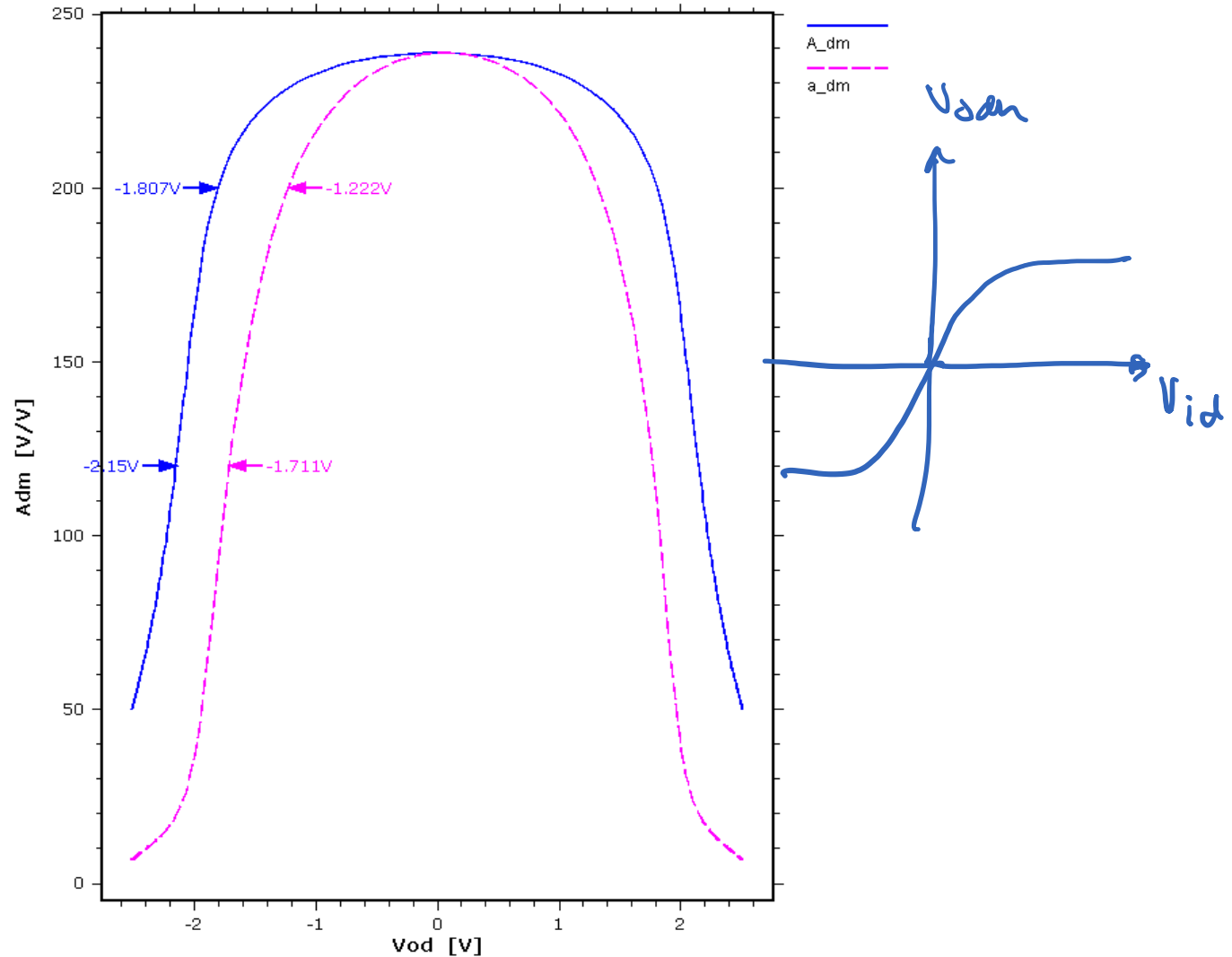


Output Resistance

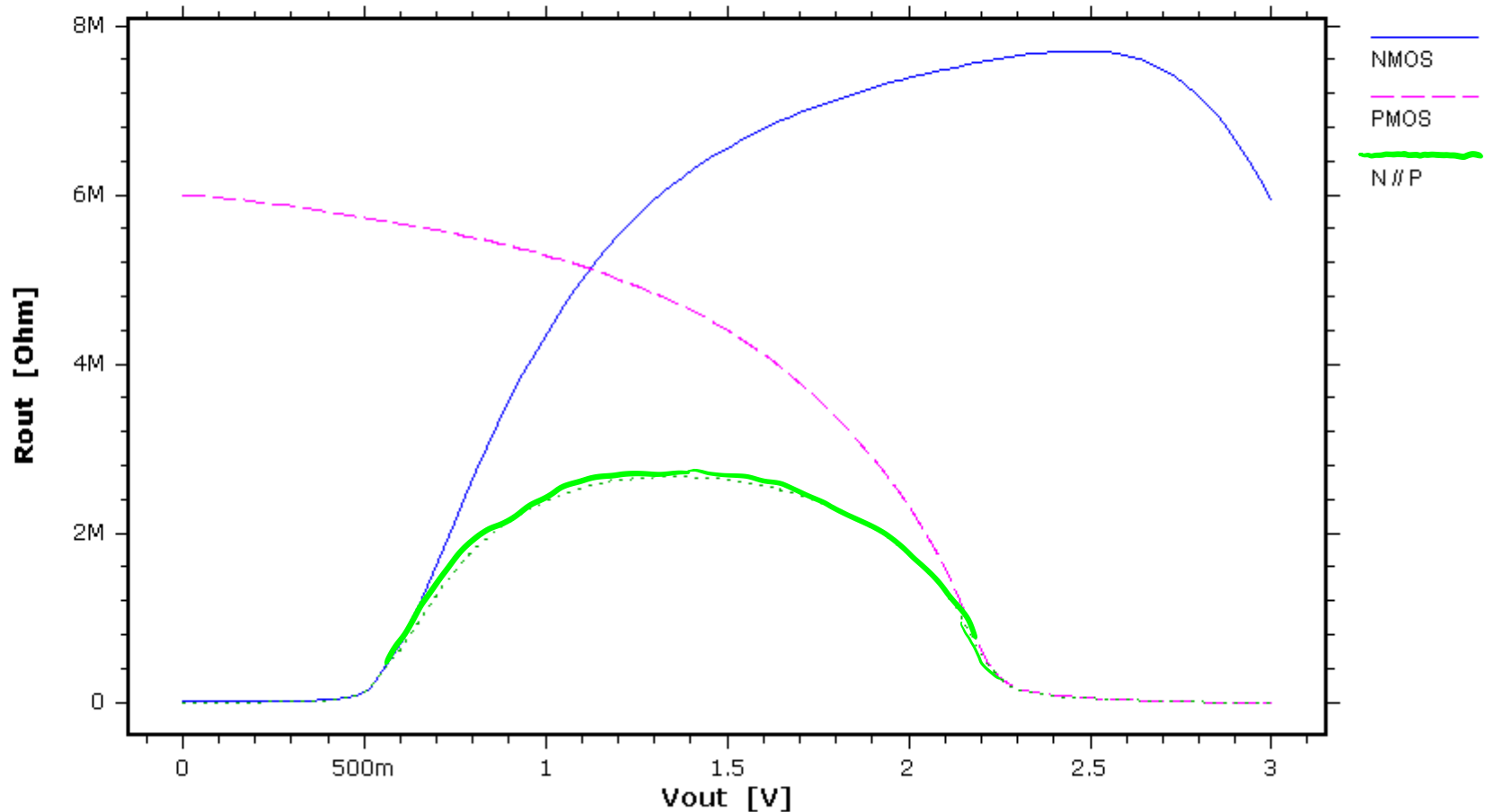


Beware of r_o imbalance between NMOS and PMOS current sources


Simulation Schematic

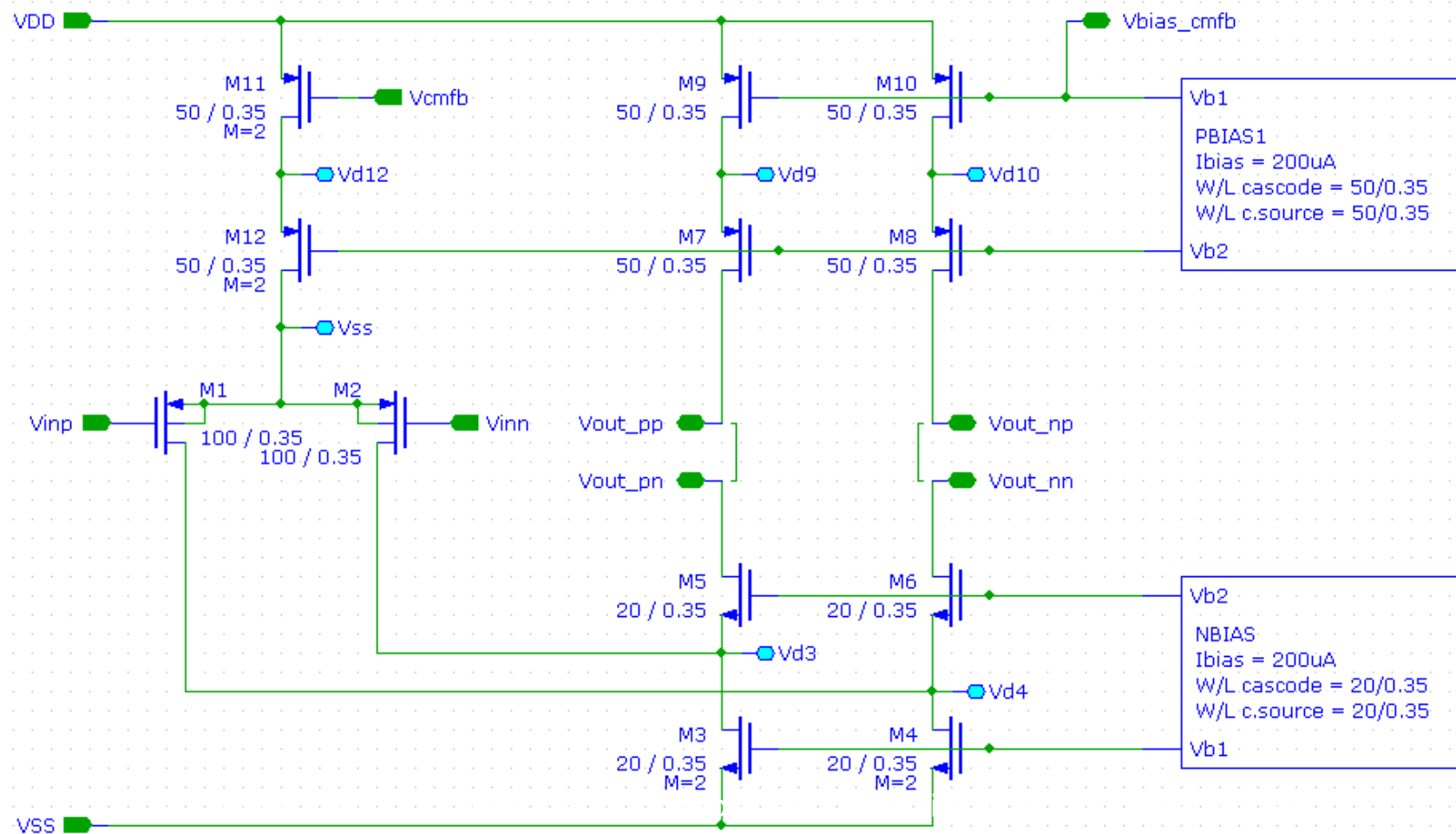

Input Cascode

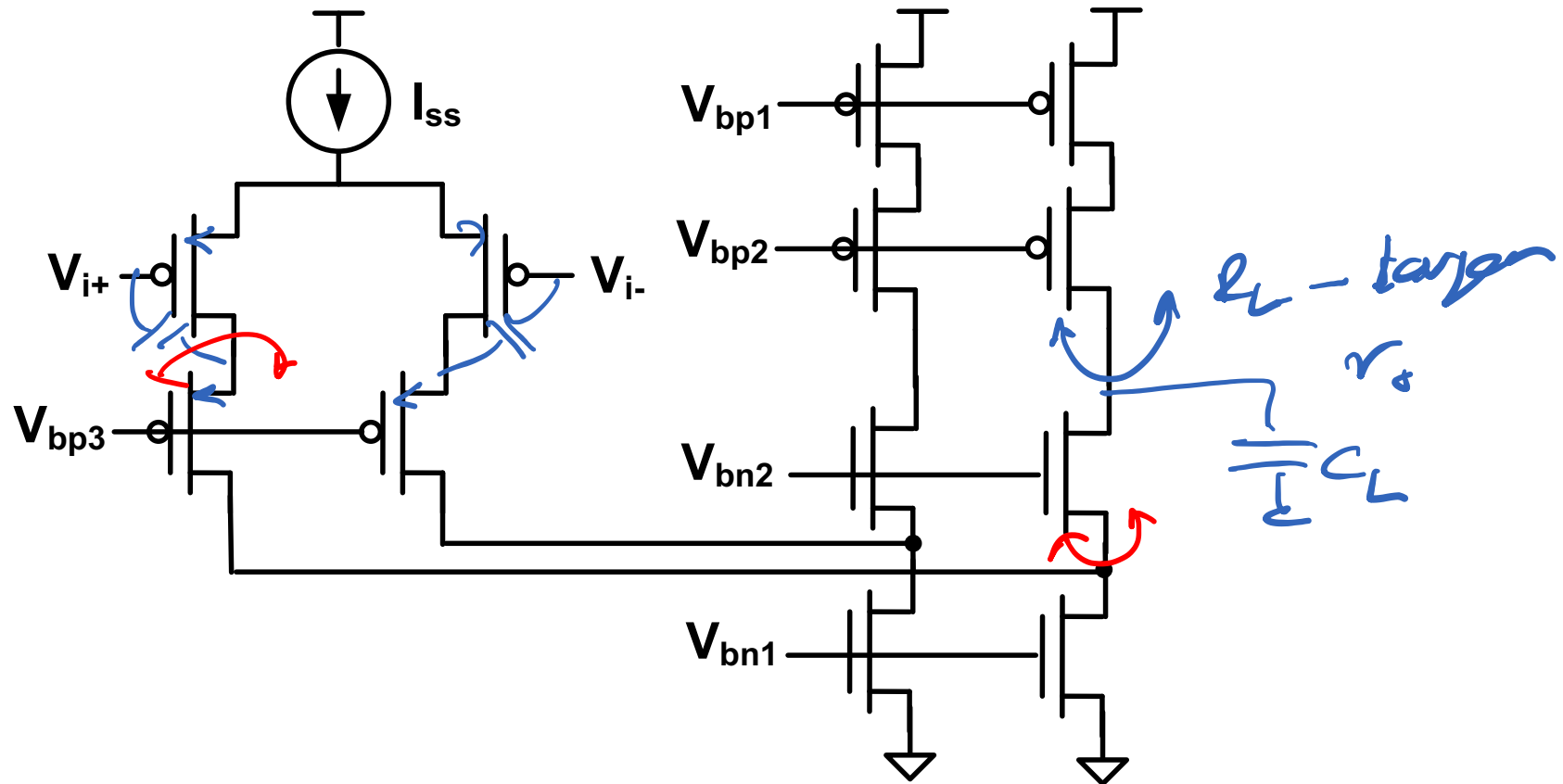


Reminder: Cascode Zin

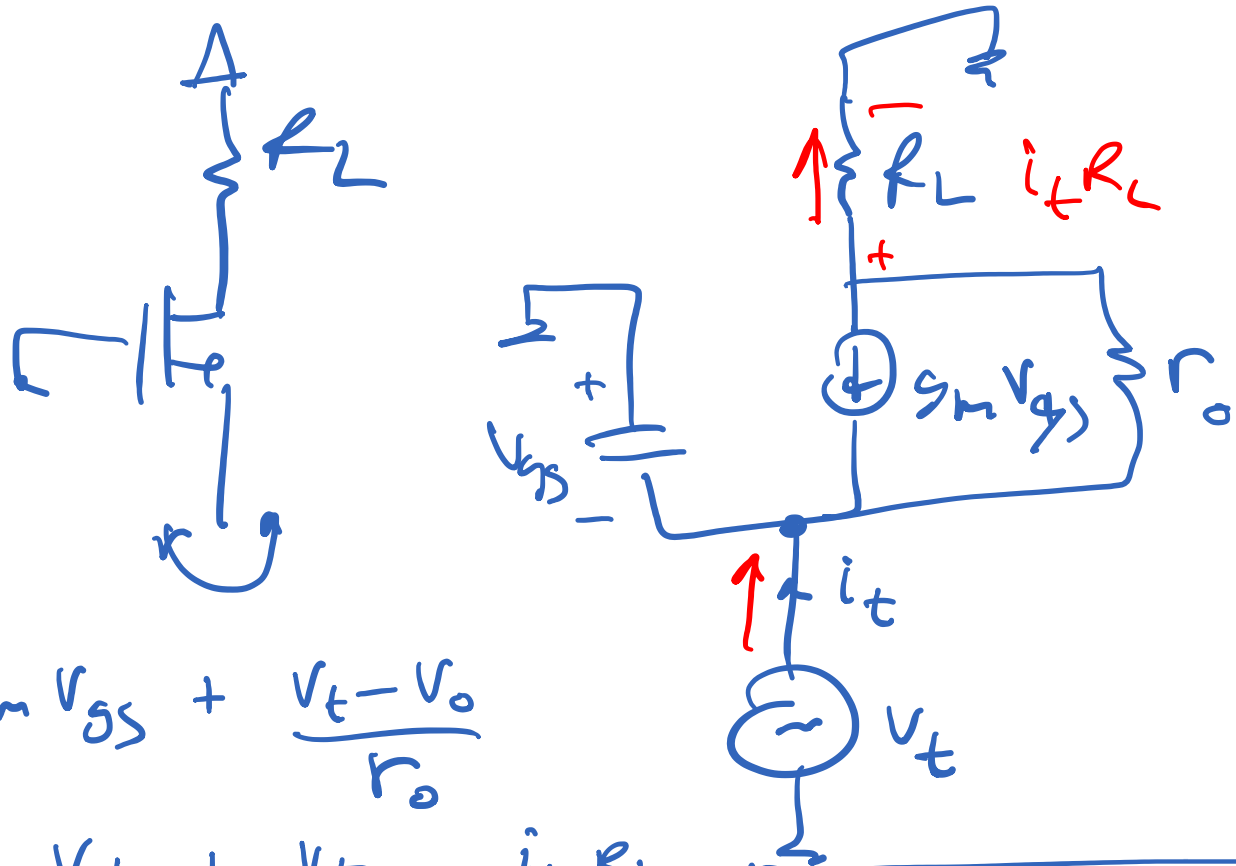

$$\begin{aligned}
 i_t &= -g_m V_{GS} + \frac{V_t - V_o}{r_o} \\
 &= g_m V_t + \frac{V_t}{r_o} - i_t \frac{R_L}{r_o} \\
 i_t \left(1 + \frac{R_L}{r_o}\right) &= \left(g_m + \frac{1}{r_o}\right) V_t
 \end{aligned}$$

$$G_{in} \approx \frac{g_m}{1 + \frac{R_L}{r_o}}$$

Biasing and Parasitic Feedback

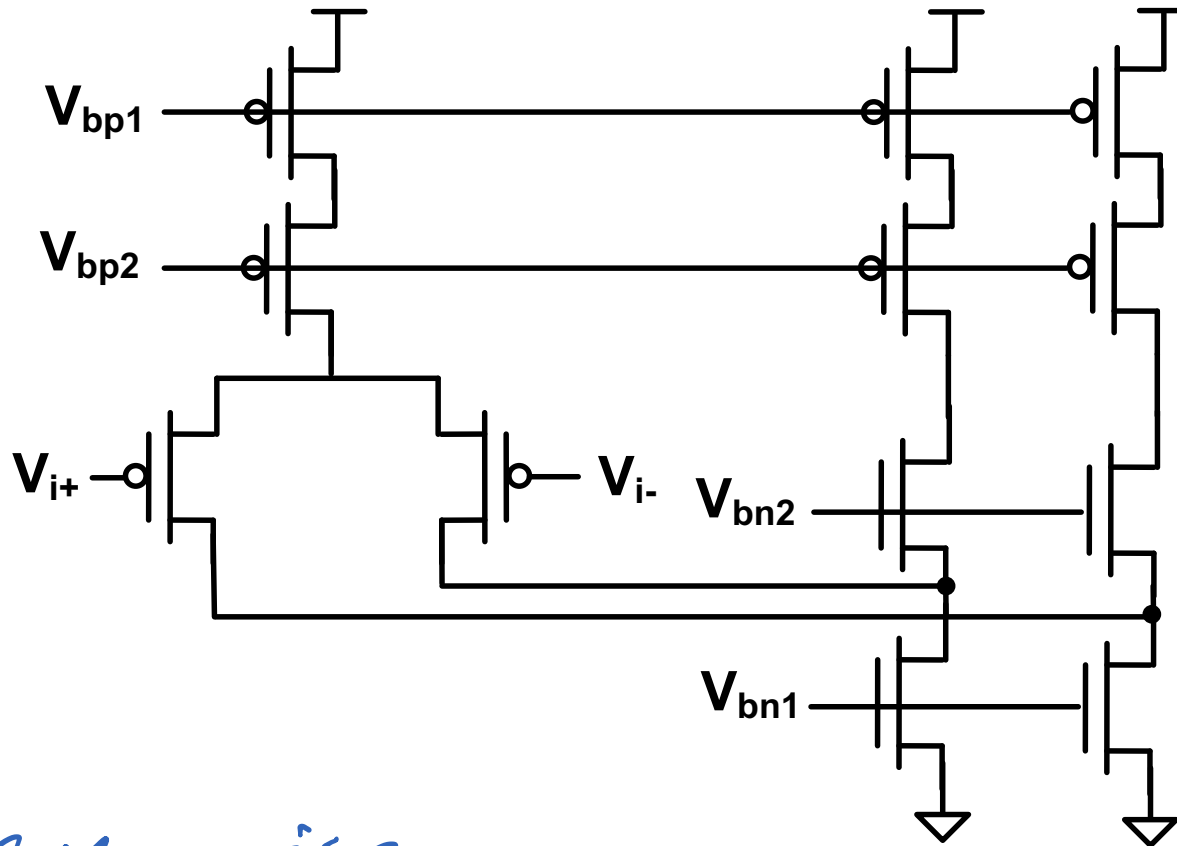

CM noise